

BJT

L1 → I-V characteristics → Input  
→ Output



$V_{CC}$  → src collector 40.5mV connected

$V_{BB}$  → base

$V_{EE}$  → emitter

\* BJT → 3 terminal device

\* 3rd terminal is for control

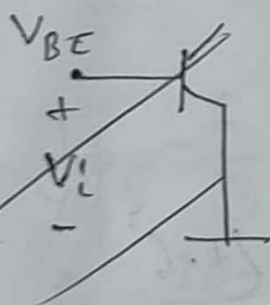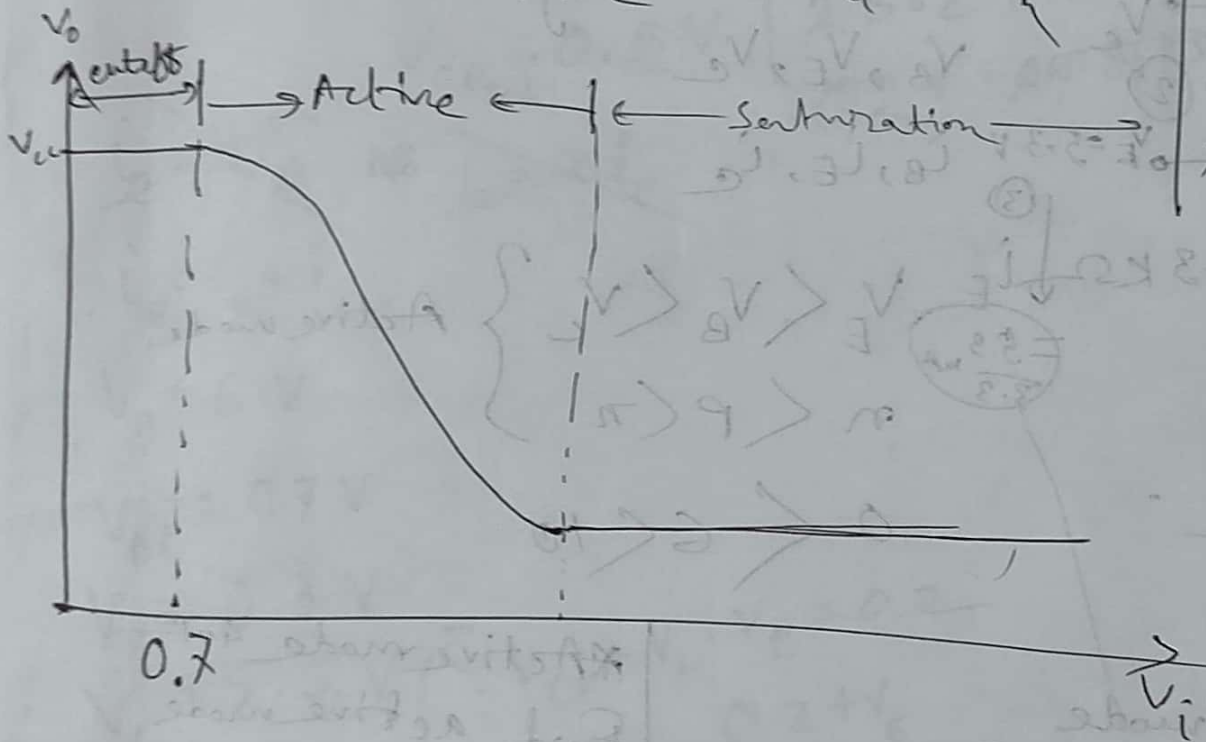

Mode of operation

Cut off

Active

Reverse Active

Saturation

E-B jnc

Rev

Fwd

Rev

Fwd

C-B jnc

Rev

Rev

Fwd

Fwd

Fwd = Forward Biased


Rev = Reverse "

Transistor Resistor = Transistor

→ BJT (Bipolar Junction Transistor)  
→ FET (Field Effect Transistor)

For BJT: (Or Vacuum Tube use  $\pi$  or  $2\pi$ )

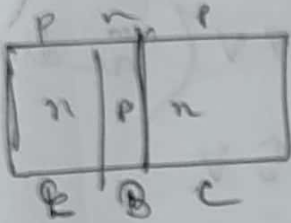\* 2 charge carrier  $\rightarrow$  Majority  
Minority



for amplifier: Fwd. Active/Active  
&  
Reverse Active  
mode  $\rightarrow$  (Forward Active mode)

Switch  $\rightarrow$  Saturation & Cut off mode

Basic Circuit Configs:

① CE ② CB ③ CC  $\rightarrow$  dummy, buffer. (i/p  $\rightarrow$  i<sub>B</sub>  
o/p  $\rightarrow$  i<sub>E</sub>)


$\rightarrow$  CE = Common Emitter Config

CB = Base

CC = Collector

i/p: base input current (unless CB config)

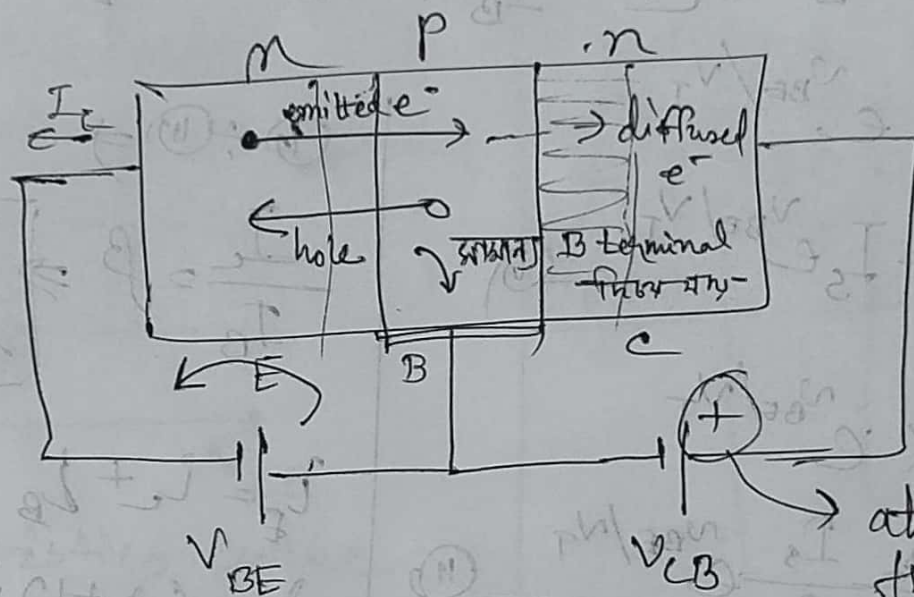o/p: collector current (unless CC config)



attracts  
the  $e^-$  of base  
emitted  
from E

$N_{\text{eff}}$  ,  $\left( \begin{array}{c} \leftarrow \\ \leftarrow \\ \rightarrow \end{array} \right)$

Q. 2. Let  $\alpha$  strong to  $h^t$  neutralized  $\alpha$  (17) (2)  $\therefore$

২.  $h^+$  চার্জ (সিদ্ধান্ত) : Base (২৬)  $h^+$  আয়ন।

(hence  $I_B$ )

\* We want  $I_c \uparrow \therefore$  base width  $\downarrow$ , collector width  $\uparrow$

\*  $V_{CB} \uparrow$  depletion region (of B-C jnc)  $\uparrow$

for this base width ↓, base doping ↓

↳ to reduce recombination

So that electrons  
don't wear out



$$\therefore I_E = I_B + I_C \quad I_B \ll I_C \therefore I_E \approx I_C \quad \left[ \text{Sometimes assumed} \right]$$

$$I_C \propto e^{V_{BE}/V_T}$$

$$\Rightarrow I_C = I_S e^{V_{BE}/V_T} \quad (i)$$

$$I_B \propto e^{V_{BE}/V_T}$$

$$\Rightarrow \frac{I_C}{I_B} = \frac{I_S}{I_S} e^{V_{BE}/V_T} = \beta \quad (ii)$$

$\alpha = \frac{C B}{C E}$  current gain

$\beta = \frac{C E}{C B}$  current gain

CB = Common Base

CE = Common Emitter

$$\frac{I_C}{I_B} = \beta \Rightarrow \beta = \frac{I_C}{I_B}$$

$$\boxed{\beta = \frac{I_C}{I_B}}$$

$$I_E = I_C + I_B$$

$$\Rightarrow I_E = (\beta + 1) I_B$$

$$\therefore I_E = \left( \frac{\beta + 1}{\beta} \right) I_C$$


$$\Rightarrow I_E = \frac{I_C}{\alpha} \quad \left| \quad \alpha = \frac{\beta}{\beta + 1} \right. \quad (\text{defn})$$

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E + I_{CO}$$

Reverse Saturation current (CB junction)

$I_{CO} \rightarrow$  can be ignored

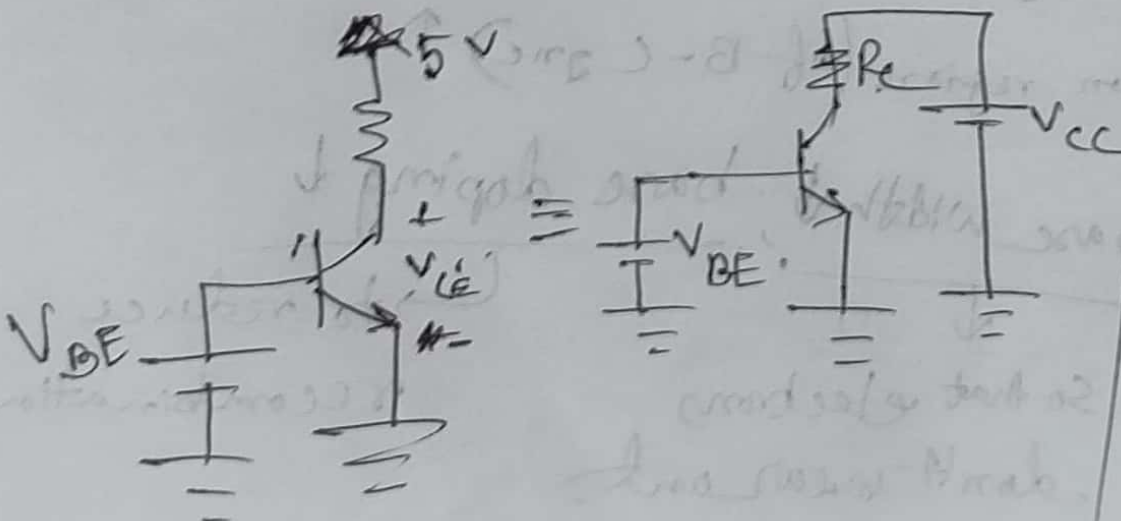

## Saturation Mode:

$\vec{E}$  = electric field

threshold voltage:

$$V_{BE} = 0.7V \quad (\text{for diodes})$$

$$V_{BE} = 0.5V$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$= -V_{BE} + V_{BE}$$

$$= (-0.5 + 0.7)V = 0.2V$$

$\therefore (V_{CE})_{sat} = 0.2V \rightarrow$  for

practical problems

\*  $V_{BE} = \text{const} = 0.7V$ ,  $V_{CE}$  change and  $i_E$  emitter current

base  $\rightarrow$  more attractive  $\vec{E}$  face and  $\therefore i_E$  will be attracted towards  $e$ .  $\vec{E} \uparrow$  with the increase of  $V_{CE}$ ,  $\therefore i_E \downarrow$

$$\beta = \frac{i_C}{i_B}$$

$$i_C \downarrow \beta \downarrow \text{ and } i_B$$

$\therefore$  so  $\beta \neq \text{const}$ ,  $\beta$  is forced to decrease.


Pr 1:

+10 V

Calculate all mode voltages and current.

For active mode, assume

$$\beta = 100$$

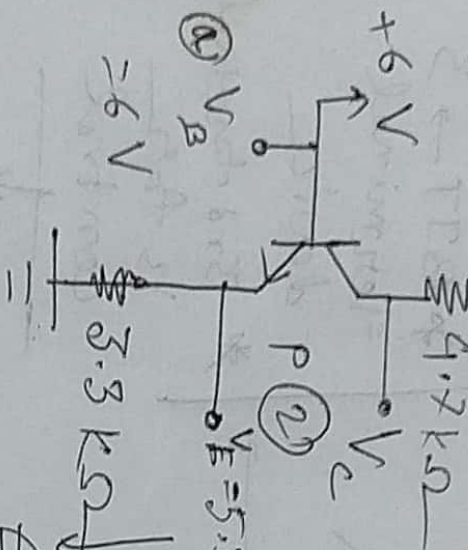

$$V_B, V_E, V_C$$

$$I_B, I_E, I_C$$

$$\left. \begin{array}{l} V_E < V_B < V_C \\ n < p < n \end{array} \right\} \text{Active mode}$$

$$0 < \beta < 10$$

Assume,

active mode

$$V_{BE} = 0.7 \text{ V}$$

Active mode and  
Find. active mode

$$I_E = \frac{5.3}{3.3} = 1.64 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1+\beta} I_E$$

$$\frac{33}{200} \frac{5.3}{3.3} (1.6)$$

$$\beta = \frac{I_C}{I_B} \Rightarrow I_B = \frac{I_C}{\beta}$$

$$\textcircled{5} V_C = 10 - 4.7 I_C = 2.48 \text{ V}$$

$$\text{we get } \rightarrow V_E < V_B < V_C$$

Assumption  
wrong



Assuming Saturation mode

$$V_E < V_B > V_C$$

$$\Rightarrow n < p \quad n$$

Assump: for sat. mode:

$$V_{CE_{sat}} = 0.2 \text{ V}$$

$$[2.682 \text{ find bias } \rightarrow \text{ mode}]$$

~~$$i_B = \beta i_C$$~~

~~$$i_C = \alpha i_E$$~~

$$i_E = i_B + i_C$$

$$V_B = 6 \text{ V}$$

$$V_{BE} = 0.7 \text{ V}$$

$$V_E = 5.3 \text{ V}$$

$$V_C = 5.5 \text{ V}$$

$$\because V_{CE} = V_C - V_E = 0.2 \text{ V}$$

$$V_C = 0.2 + V_E$$

$$i_E = \frac{5.3}{3.3} = 1.6 \text{ mA}$$

$$= (5.5 \text{ V})$$

$$i_C = \frac{10 - 5.5}{4.7} = 0.96 \text{ mA}$$

$$i_B = i_E - i_C = 0.64 \text{ mA}$$

$$\beta_{forced} = \frac{i_C}{i_B} = \frac{0.96}{0.64} = 1.5$$


$\hookrightarrow$  sat. mode  $\Rightarrow \beta$  (sat. mode)  $\approx 1$

Pr2 |:

Calculate all node voltages & current.

For active mode, assume

$$\beta = 100.$$

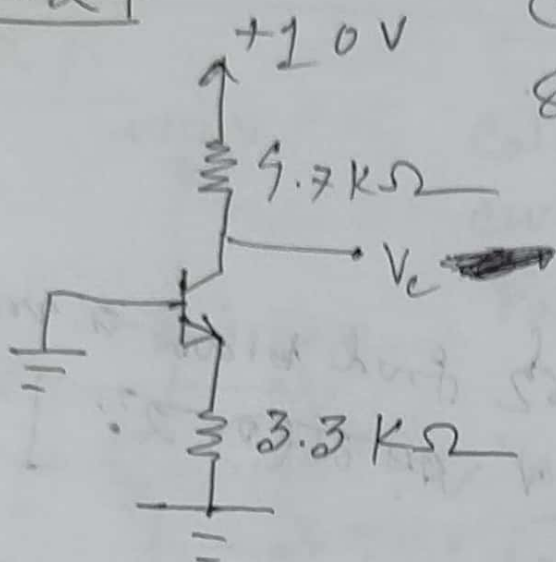

Ans:  $V_E < V_B < V_C$   
n

\* Assumption for active mode:  
+10V  
0V  
0V

$V_E$	$V_B$	$V_C$
n	p	n
0	0	10
Rev	Rev	

\* Active mode error:

(Not a circuit)

assess current direction

assumption check for error

$$I_E = I_B = I_C = 0 \text{ A}$$

$$V_C = +10 \text{ V}$$


$$V_B = 0 \text{ V}$$

$$V_E = 0 \text{ V}$$

Pr3



Pr 3]

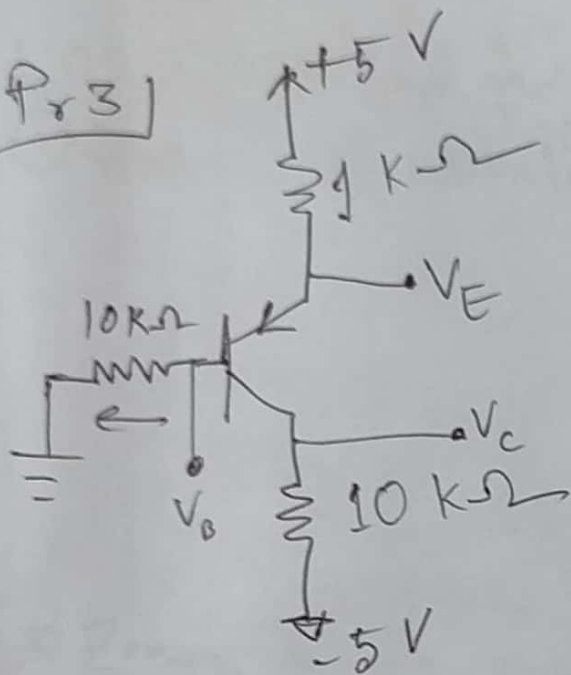

Calculate all node voltages and current.

For active mode, assume  $\beta = 100$

Ans: Assuming saturation mode

$$V_{CE\text{ sat}} = 0.2 \text{ V}$$

⇒ Assuming active mode:

$i_B$  very small ( $\mu\text{A}$  range)

$$\therefore V_B \approx 0 \text{ V}$$

$$V_E = 0.7 \text{ V} \quad [\because V_{BE} \approx 0.7 \text{ V}]$$

$$i_E = \frac{5 - 0.7}{1} = 4.3 \text{ mA}$$

$$\therefore i_C \approx i_E \quad [\because i_B \approx 0]$$

$$\therefore V_C = 10i_C - 5$$

$$= 43 - 5 = 38 \text{ V}$$

Now,

E	B	C
P	N	P
0.7	0	38

$\overline{Fwd.}$   $\overline{Fwd.}$

∴ Assumption was wrong


~~Ans~~

Assume saturation mode

$$V_{EC\text{ sat}} = 0.2 \text{ V} \quad | \quad i_E = i_B + i_C$$

$$V_{EB} = 0.7 \text{ V} \quad | \quad i_E = \frac{5 - V_E}{1 \text{ k}\Omega} = (5 - V_E) \text{ mA}$$

Current dir:

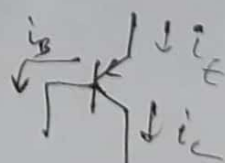

$$5 - (V_B + 0.7)$$

$$i_B = \frac{V_B}{10} \text{ mA}$$

$$\Rightarrow \frac{V_B}{10} + \frac{V_B + 0.5 + 5}{10} \quad \left[ i_E = i_B + i_C \right]$$

∴

$$i_C = \frac{V_C + 5}{10} = \frac{V_B + 5.5}{10} \text{ mA}$$

$$i_E = i_B + i_C$$


$$\Rightarrow \frac{V_B}{10} + 5 - V_E = \frac{V_B}{10} + \frac{V_B}{10} + \frac{5.5}{10}$$

$$\Rightarrow 5 - 0.7 - V_B = 0.2V_B + 0.55$$

$$\Rightarrow V_B = \boxed{\phantom{00}} \text{ V}$$

?

[ANALYSIS class missed]

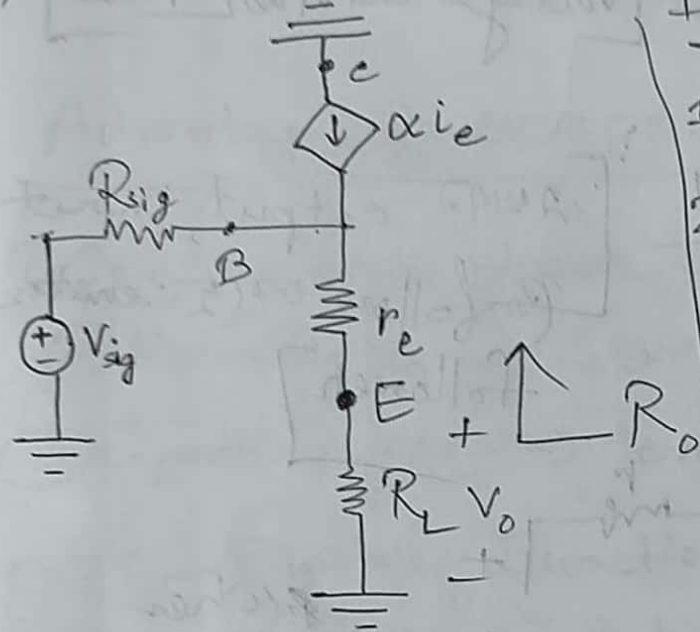


Derive:

- 1)  $R_{in}$  ①  $R_{in} = (\beta + 1)(r_e + R_L)$
- 2)  $R_o$
- 3)  $A_v$
- 4)  $A_{v_o}$
- 5)  $G_v$

①  $R_{in} = (\beta + 1)(r_e + R_L)$

②  $R_o$  (to find  $R_o$ ):

$V_i$  is shorted,  $V_i = V_{sig} = 0$

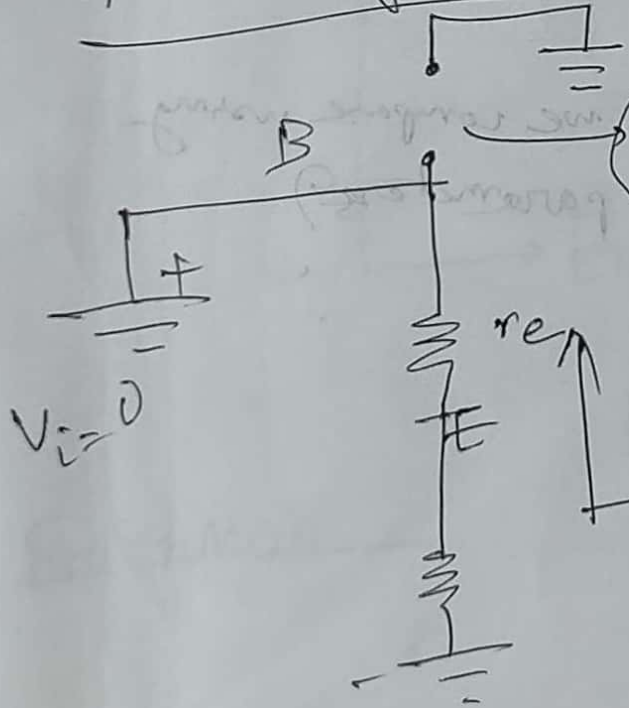

Current source to open ckt ( $I = 0$ )

2 terminals  $\rightarrow$  ground

$\therefore \Delta V = 0 - 0 = 0$

$\therefore R_o = r_e$

Self Study

CE Amplifier

CE

with Emitter Resistance



Sedra & Smith

Derive Expressing



$$(ii) A_v = \frac{v_o}{v_i} = \frac{R_L}{r_e + R_L} \quad [\text{voltage divider rule}]$$

$$(iii) A_{v_o} = A_v \Big|_{R_L \rightarrow \infty} = 1 \quad \left[ \begin{array}{l} \text{max output, input} \\ \text{to follow } v_i \text{ (} \therefore \text{ emitter} \\ \text{follower} \end{array} \right]$$

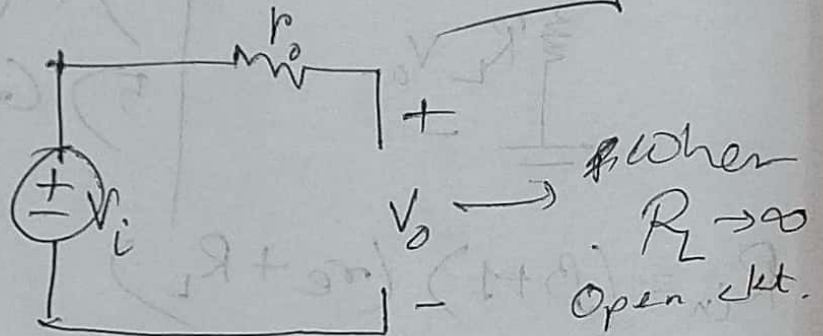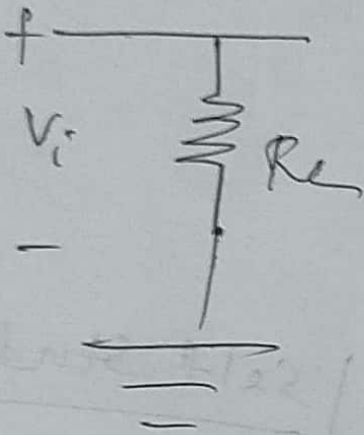

THINK:

Why will we use

① CC/Emitter follower?

② Input resistance?

③ Output "

How do we compare using these parameters?

[BJT Done]